

DC Amplifier

Buereddy Varuni*

A DC amplifier has an open loop gain of 1000 and two poles, a dominant one at 1kHz and a high frequency one whose location can be controlled. It is required to connect this amplifier in a negative feedback loop that provides a DC closed loop gain of 10 and a maximally flat response.

1. Find the required value of H .

Solution: Table 1 summarises the given information. The open loop gain can be expressed as

$$G(s) = \frac{G_0}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)} \quad (1.1)$$

$$\Rightarrow G(0) = G_0 \quad (1.2)$$

The closed loop gain

$$T(s) = \frac{G(s)}{1 + G(s)H} \quad (1.3)$$

$$\Rightarrow T(0) = \frac{G_0}{1 + G_0H} \quad (1.4)$$

Substituting from Table 1,

$$\frac{1000}{1 + 1000H} = 10 \quad (1.5)$$

$$\Rightarrow H = 0.099 \quad (1.6)$$

Parameter	Value
dc open loop gain	1000
dominant pole	-1000Hz
insignificant pole	$-p_2$
dc closed loop gain	10

TABLE 1: 1

$$G_0 = 1000 \quad (1.7)$$

$$\text{Therefore, } G(s) = \frac{1000}{\left(1 + \frac{s}{p_1}\right)\left(1 + \frac{s}{p_2}\right)} \quad (1.8)$$

2. Find p_2 .

Solution: From (1.3) and (1.1),

$$T(s) = \frac{p_1 p_2 G_0}{s^2 + (p_1 + p_2)s + (HG_0 + 1)p_1 p_2} \quad (2.1)$$

$$= \frac{K\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2} \quad (2.2)$$

$$\omega_n = \sqrt{(HG_0 + 1)p_1 p_2}$$

$$\Rightarrow \zeta = \frac{p_1 + p_2}{2\sqrt{(HG_0 + 1)p_1 p_2}} \quad (2.3)$$

using the standard formulation for a second order system. Also, for maximally flat response, the quality factor

$$Q = \frac{1}{2\zeta} = \frac{1}{\sqrt{2}} \quad (2.4)$$

$$\Rightarrow \zeta = \frac{1}{\sqrt{2}} \quad (2.5)$$

$$\Rightarrow \frac{p_1 + p_2}{2\sqrt{(HG_0 + 1)p_1 p_2}} = \frac{1}{\sqrt{2}} \quad (2.6)$$

$$\Rightarrow \sqrt{\frac{p_1}{p_2}} + \sqrt{\frac{p_2}{p_1}} = \sqrt{2(HG_0 + 1)} \quad (2.7)$$

The above equation is of the form

$$x + \frac{1}{x} = a \quad (2.8)$$

$$\Rightarrow x = \frac{a \pm \sqrt{a^2 - 4}}{2} \quad (2.9)$$

where

$$x = \sqrt{\frac{p_2}{p_1}} \quad (2.10)$$

$$a = \sqrt{2(HG_0 + 1)}, \quad (2.11)$$

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

Thus, from (2.10), (2.11) and (2.9),

$$p_2 = p_1 \left[\frac{\sqrt{2(HG_0 + 1)} \pm \sqrt{2(HG_0 + 1) - 4}}{2} \right]^2 \quad (2.12)$$

From the following code,

```
codes/ee18btech11005/ee18btech11005_1.py
```

$$p_2 = 1244038.9567529503 \quad \text{and } 31.734068607786863 \quad (2.13)$$

3. Draw the equivalent circuit system diagram.

Solution: The equivalent circuit system is shown in the figure.3

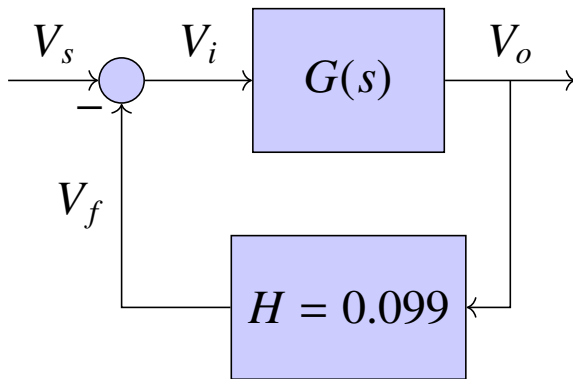


Fig. 3: 1

4. Obtain $G(s)$ and $T(s)$

Solution: Substituting the value of p_2 in (1.1) and (2.1),

$$G(s) = \frac{1000}{(1 + \frac{s}{2\pi 10^3})(1 + \frac{s}{1.244 \times 10^6})} \quad (4.1)$$

$$T(s) = \frac{10}{0.128 \times 10^{-11} s^2 + 1.599 \times 10^{-6} s + 1} \quad (4.2)$$

5. Verify from the Bode plot of above closed loop transfer function that it has maximally flat response.

Solution: The following code generates the bode plot of the transfer function in Fig. 5.

```
codes/ee18btech11005/ee18btech11005_2.py
```

6. Find the step response of $T(s)$

Solution: The following code generates the desired response of in Fig. 6.

```
codes/ee18btech11005/ee18btech11005_3.py
```

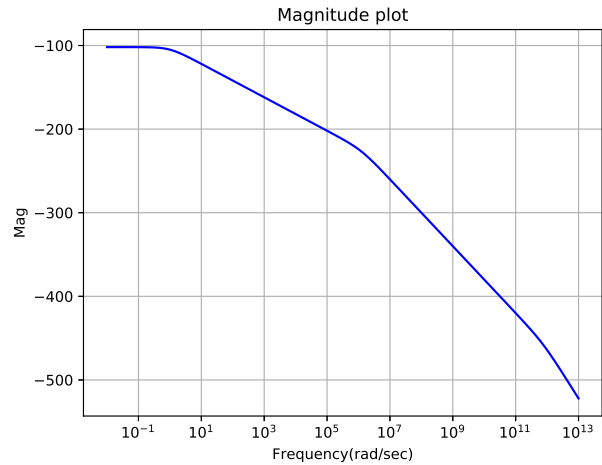


Fig. 5

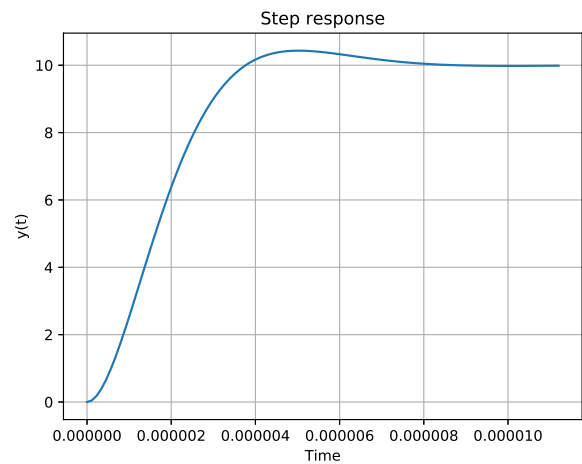


Fig. 6

7. Design a circuit that represents the above transfer function.

Solution: The circuit can be designed using operational amplifiers having negative feedback. Consider the circuit shown in figure.7:1. Assume the gain of all the amplifiers are large. And assume no zero state response. Take the parameters in s-domain.

For the first amplifier., Applying KCL at

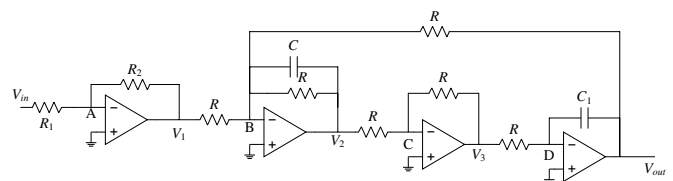


Fig. 7: 1

node A., Since, the opamp has large gain, potential at node A is assumed to be zero due to virtual short at node A.

$$\frac{0 - V_{in}(s)}{R_1} + \frac{0 - V_1(s)}{R_2} = 0 \quad (7.1)$$

$$\frac{V_{in}(s)}{R_1} = \frac{V_1(s)}{R_2} \quad (7.2)$$

$$\Rightarrow V_{in} = -\frac{V_1(s)R_1}{R_2} \quad (7.3)$$

For the second amplifier., Applying KCL at node B., Similarly potential at node B is zero.

$$\frac{-V_1(s)}{R} + \frac{-V_2(s)}{R} - sCV_2(s) + \frac{-V_{out}(s)}{R} = 0 \quad (7.4)$$

$$\frac{-V_1(s)}{R} + \frac{-V_2(s)}{R} - sCV_2(s) = \frac{V_{out}(s)}{R} \quad (7.5)$$

$$\frac{-V_1(s)}{R} = V_2(s) \left[sC + \frac{1}{R} \right] + \frac{V_{out}(s)}{R} \quad (7.6)$$

For the third amplifier., Potential at node C is zero(Due to high gain of amplifier).Applying KCL at node C.

$$\frac{-V_2(s)}{R} + \frac{-V_3(s)}{R} = 0 \quad (7.7)$$

$$\Rightarrow V_2(s) = -V_3(s) \quad (7.8)$$

For the Fourth amplifier., Potential at node D is zero.Applying KCL at node D.

$$\frac{-V_3(s)}{R} + sC_1(-V_{out}(s)) = 0 \quad (7.9)$$

$$V_3(s) = -sC_1RV_{out}(s) \quad (7.10)$$

From equation.7.10 and equation. 7.8.,

$$V_2(s) = sC_1RV_{out}(s) \quad (7.11)$$

Substituting the equation.7.6 and equation.7.11,

$$\frac{-V_1(s)}{R} = (s^2C_1CR + sC_1)V_{out}(s) + \frac{V_{out}(s)}{R} \quad (7.12)$$

$$V_1(s) = -(s^2C_1CR^2 + sC_1R + 1)V_{out}(s) \quad (7.13)$$

from equation.7.3 and equation.7.13.

$$V_1(s) = \frac{R_1}{R_2}(s^2C_1CR^2 + sC_1R + 1)V_{out}(s) \quad (7.14)$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_2}{R_1(s^2C_1CR^2 + sC_1R + 1)} \quad (7.15)$$

Comparing equation.4.2 and equation.7.15

$$\frac{R_2}{R_1} = 10 \quad (7.16)$$

$$C_1CR^2 = 0.128 \times 10^{-11} \quad (7.17)$$

$$C_1R = 1.599 \times 10^{-6} F \quad (7.18)$$

$$\text{Let., } R = 1000\Omega \quad (7.19)$$

$$\Rightarrow C_1 = 1.599 \times 10^{-9} \quad (7.20)$$

$$\text{and., } C_1CR^2 = 0.128 \times 10^{-11} \quad (7.21)$$

$$\Rightarrow C = 0.8005 \times 10^{-9} F \quad (7.22)$$

$$\text{Let., } R_1 = 100\Omega \quad (7.23)$$

$$\Rightarrow R_2 = 1000\Omega \quad (7.24)$$

From Table.7:1. The Final circuit is shown in

Parameter	Value
R_1	100 Ω
R_2	1000 Ω
R	1000 Ω
C	0.8005 nF
C_1	1.599 nF

TABLE 7: 1

figure.7

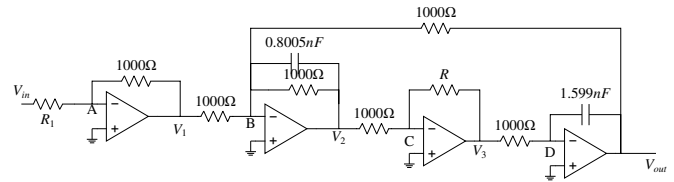


Fig. 7: 1

- Verify the closed loop DC gain using NGSPICE simulator.

Solution: The following README file gives the procedure to be followed.

codes/ee18btech11005/spice/README

From equation.4.2. The DC closed loop gain is 10.

The following netlist file, gives the DC gain of the closed loop function.

`codes/ee18btech11005/spice/gvv_ngspice.net`

We can observe from simulation that the value of DC closed loop gain is 9.997. Therefore, the value is verified using ngspice.